

# Tortoise Wiring/LED Clinic

By Bob Cochran


# Overview of what will be covered


- 1. How to wire toggle switches, LED's and frog on a turnout.
- 2. Material used.
- 3. Offset mounting/dual control

# Methods of providing changeable polarity DC


- 1. DPDT Switches
- 2. Bi-Polar DC wit SPDT Switches
- 3. AC with Steering Diodes


# BI-Polar DC

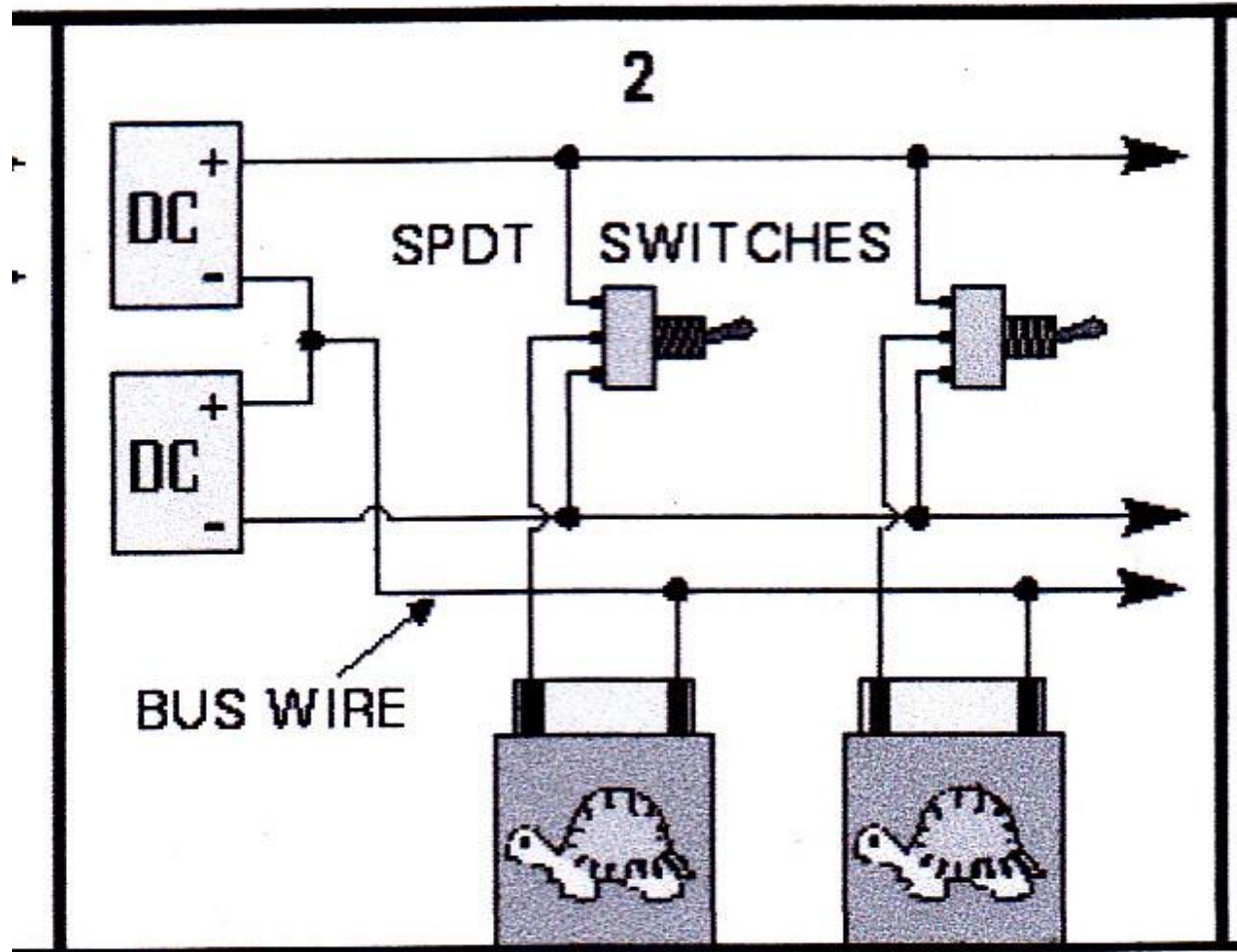

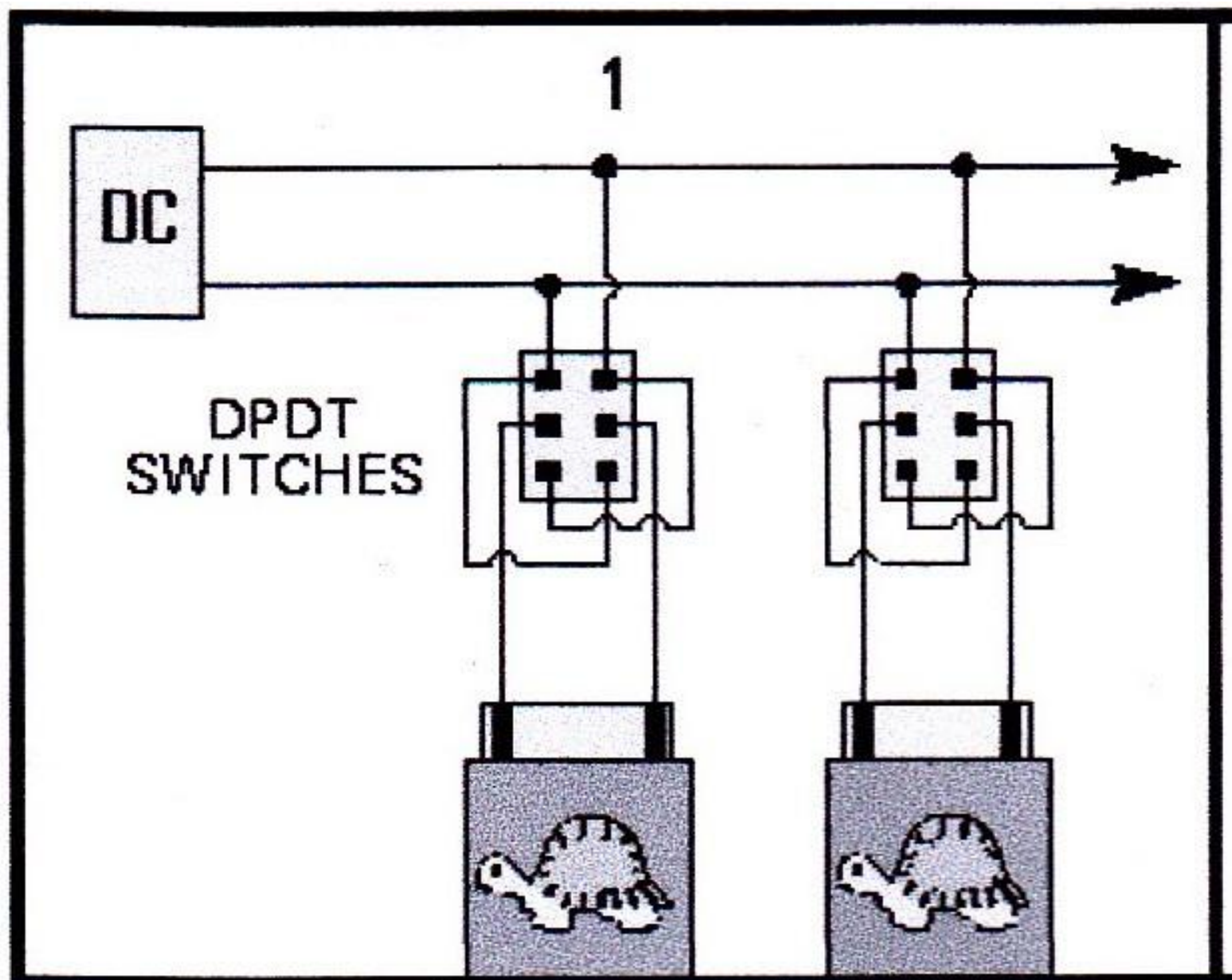

# AC with Steering Diodes

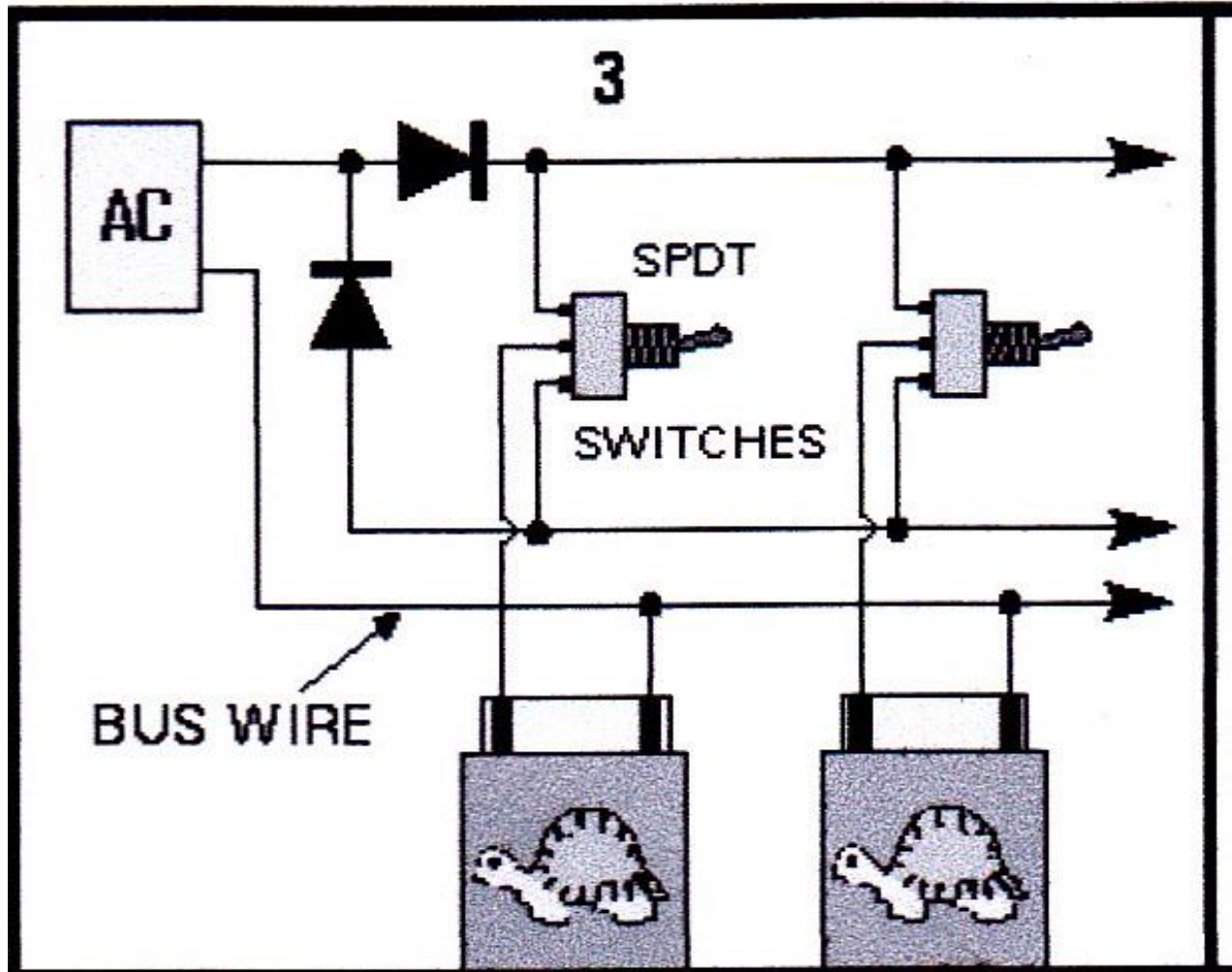

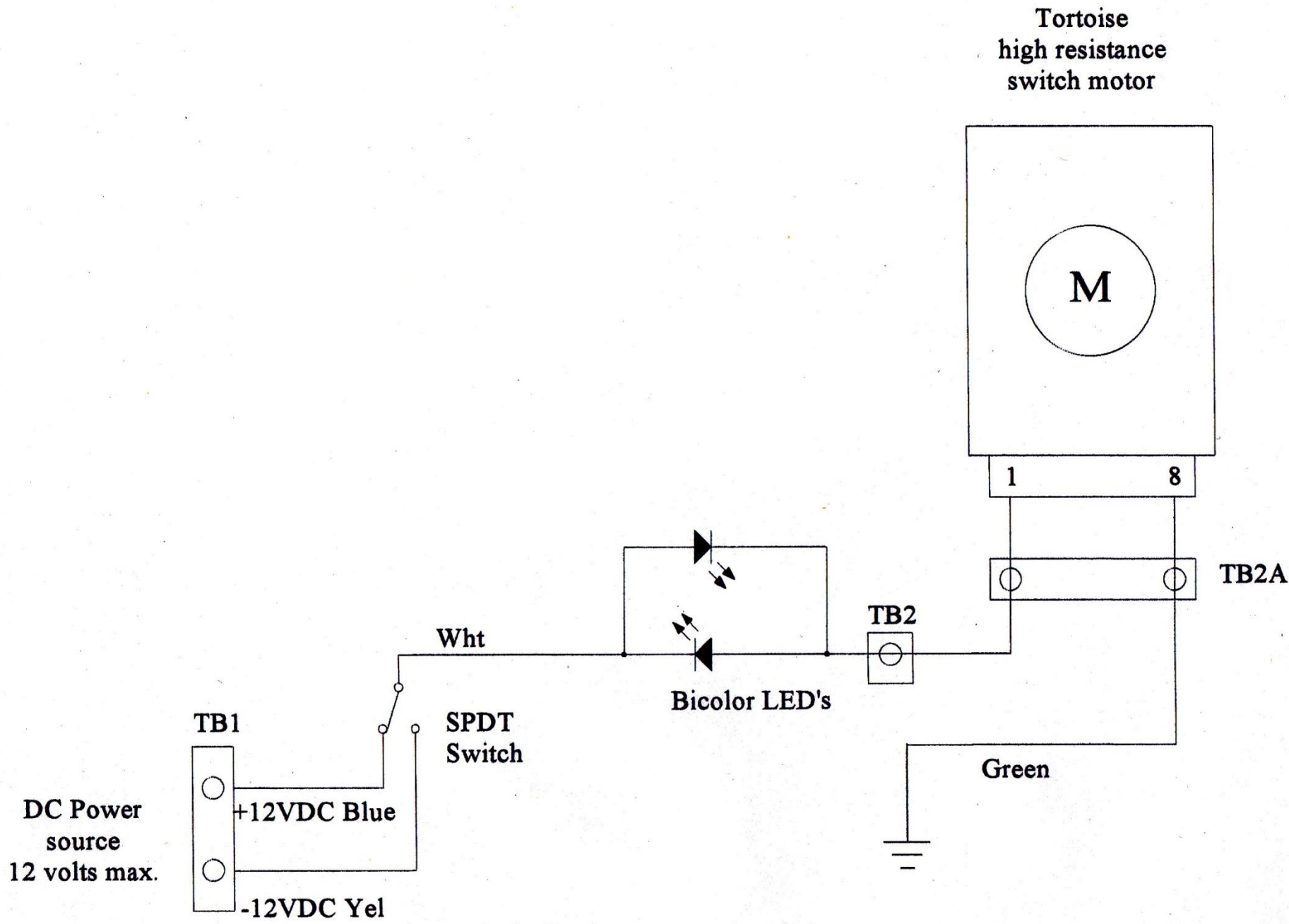



# Panel lights/Signals


- Can use 1 each red and green LED
  - Green in normal route
  - Red in diverting route
- One Bi Color LED green/red
  - In the normal route
  - Have to use 2 single LED's or 1 Bi Color LED if you are going to use Led's




4

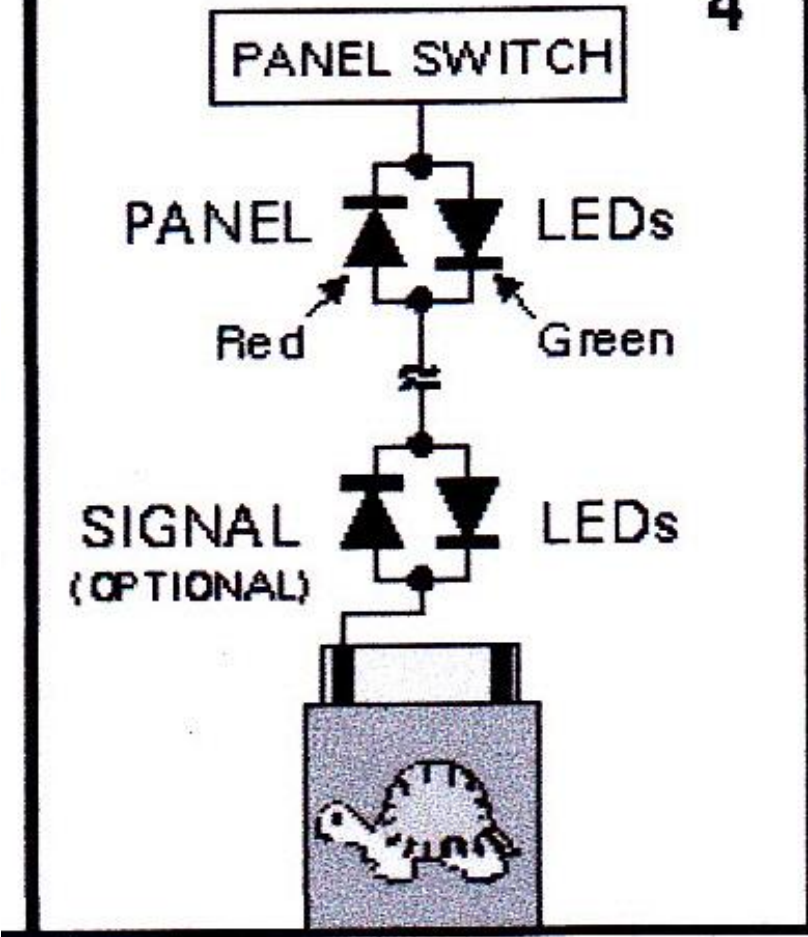

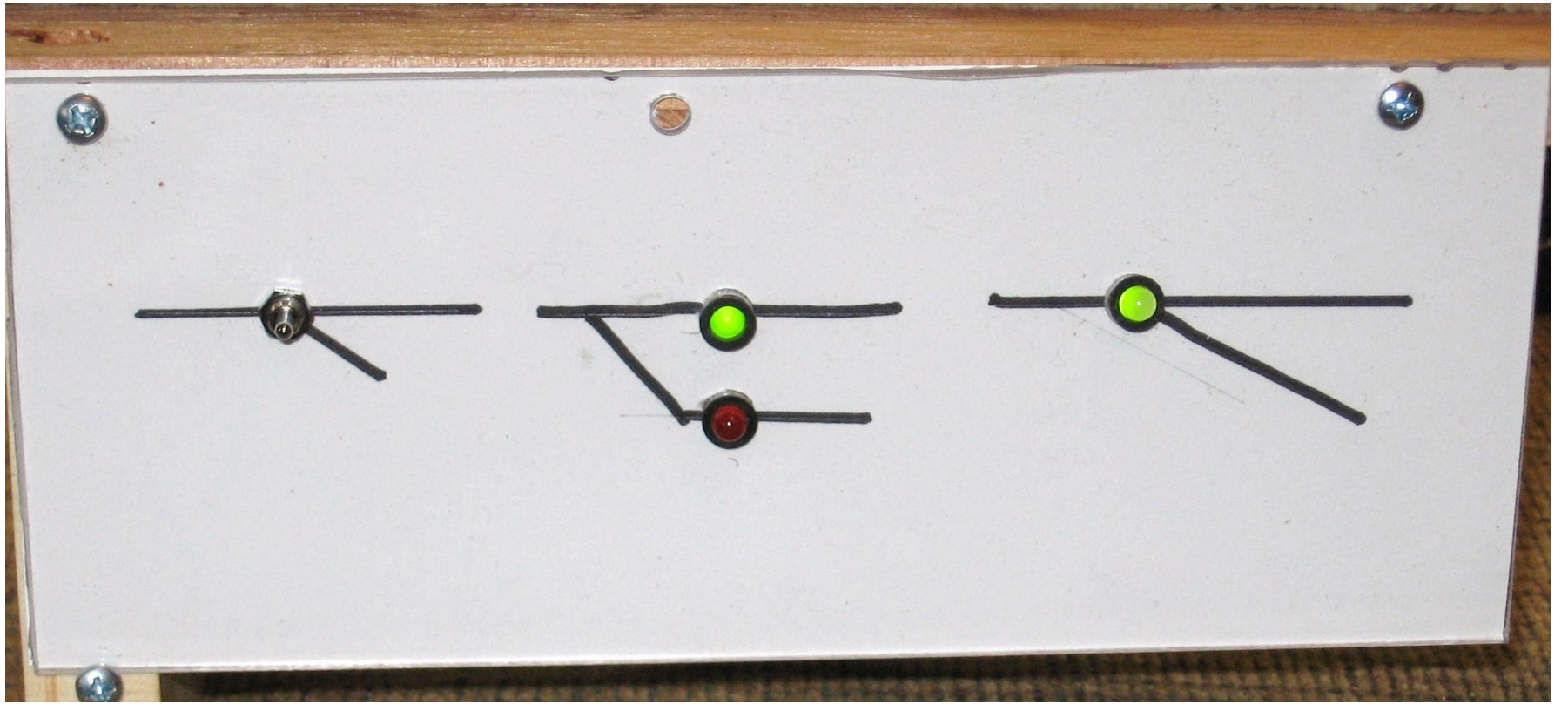


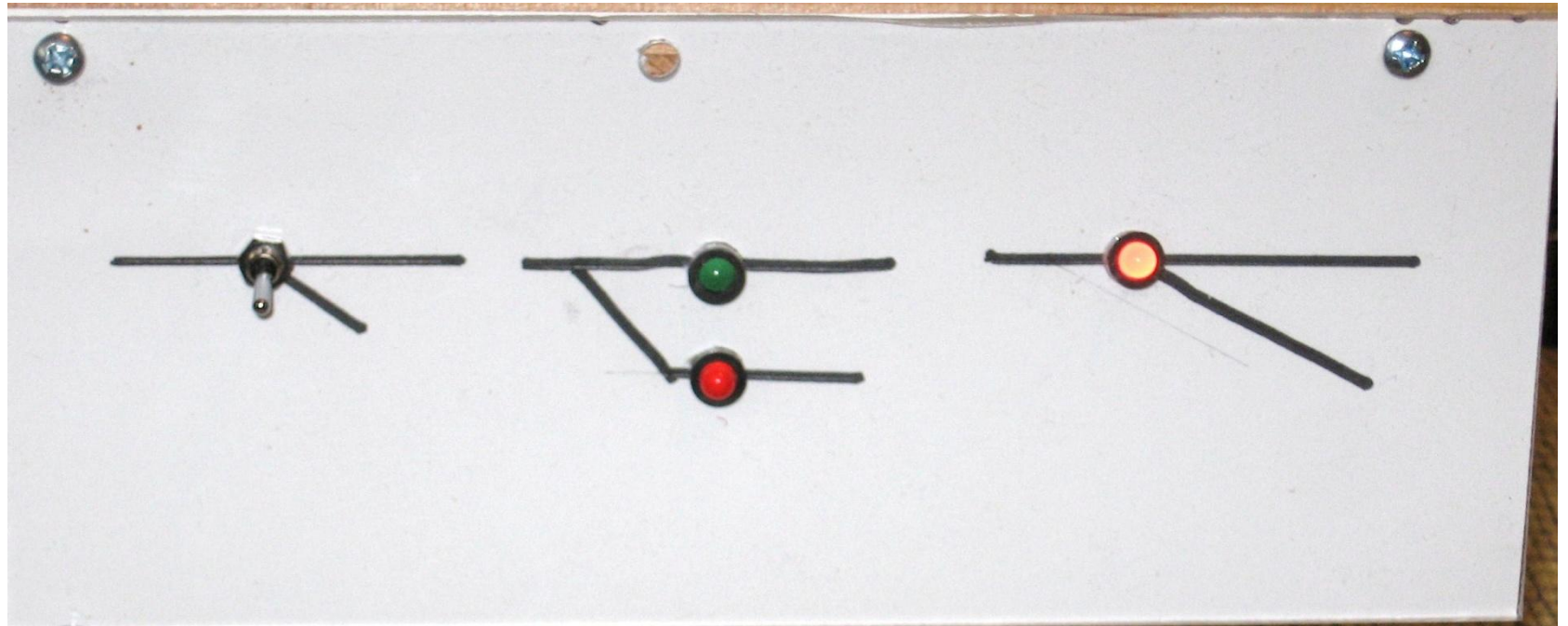



Red LED

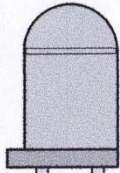

Green LED

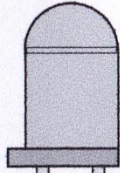

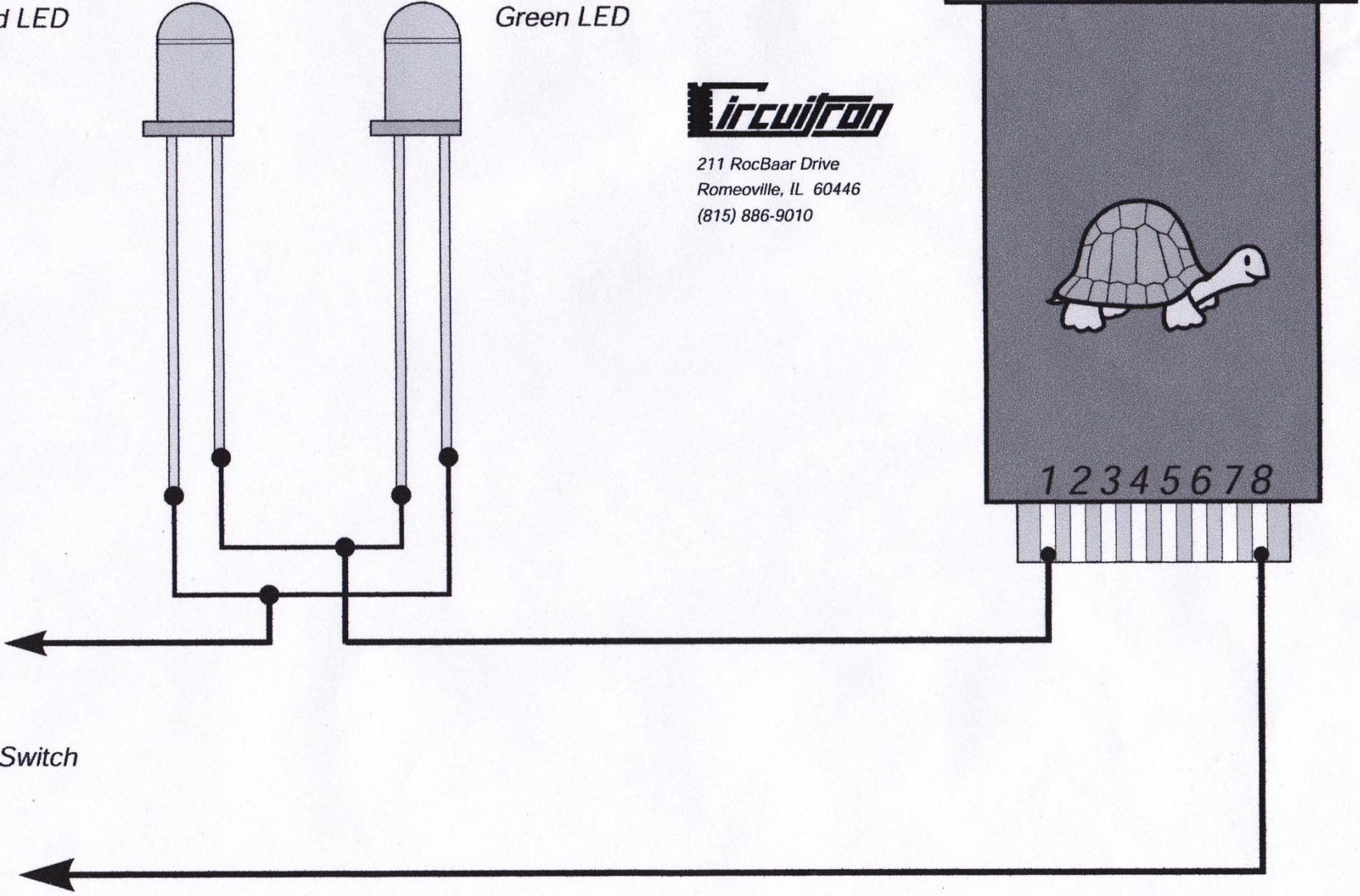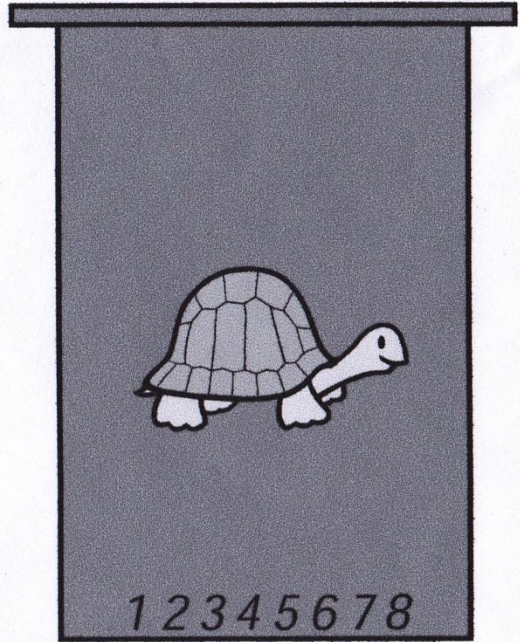211 RocBaar Drive  
Romeoville, IL 60446  
(815) 886-9010




To Panel Switch

Note: Do not use additional resistors. The resistance of the TORTOISE motor is about 600 ohms, an ideal limiting resistance for LEDs.

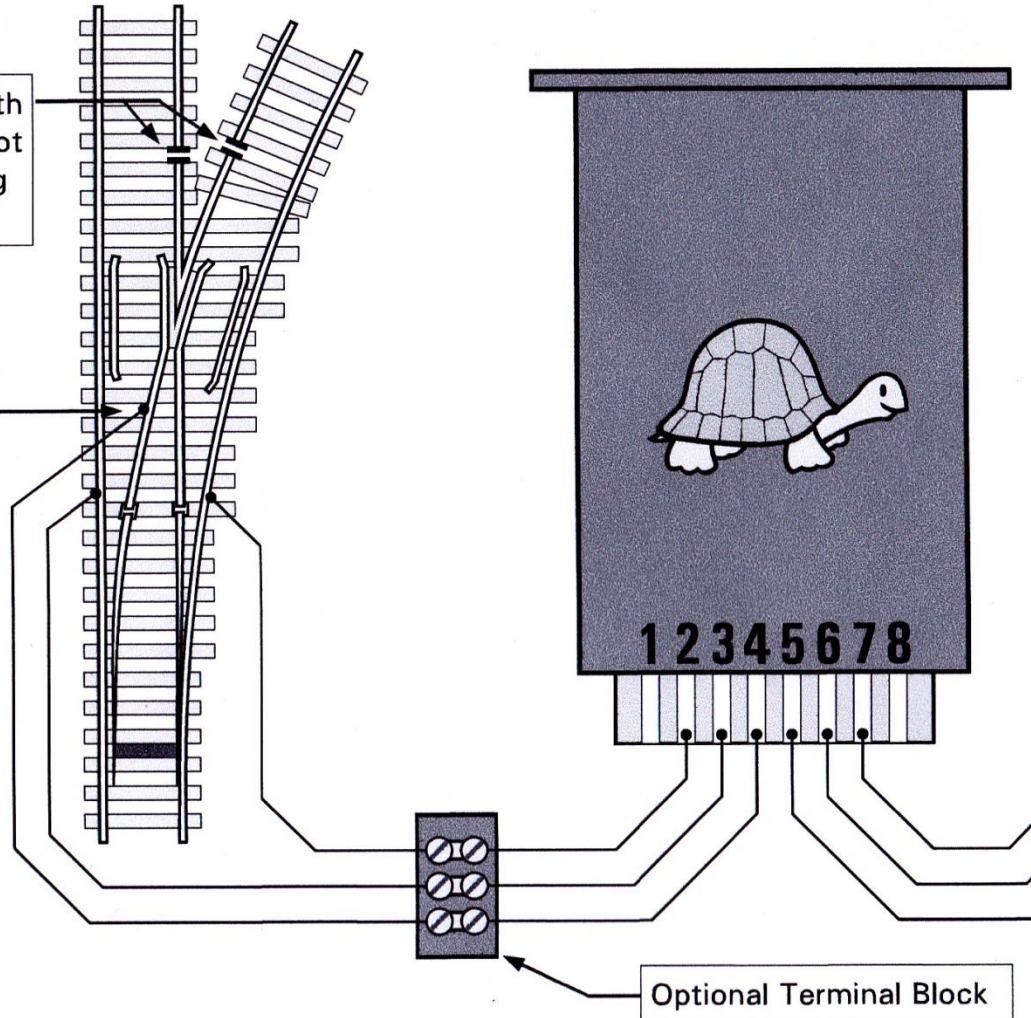
# Frog Wiring

Rail breaks necessary with "live" frog turnouts. Not needed with insulated frog (Atlas, etc.)

If you wish to power *just* the frog, this connection would be to the frog only (useful for turnouts that have the points already factory wired to the stock rails)



Optional Terminal Block

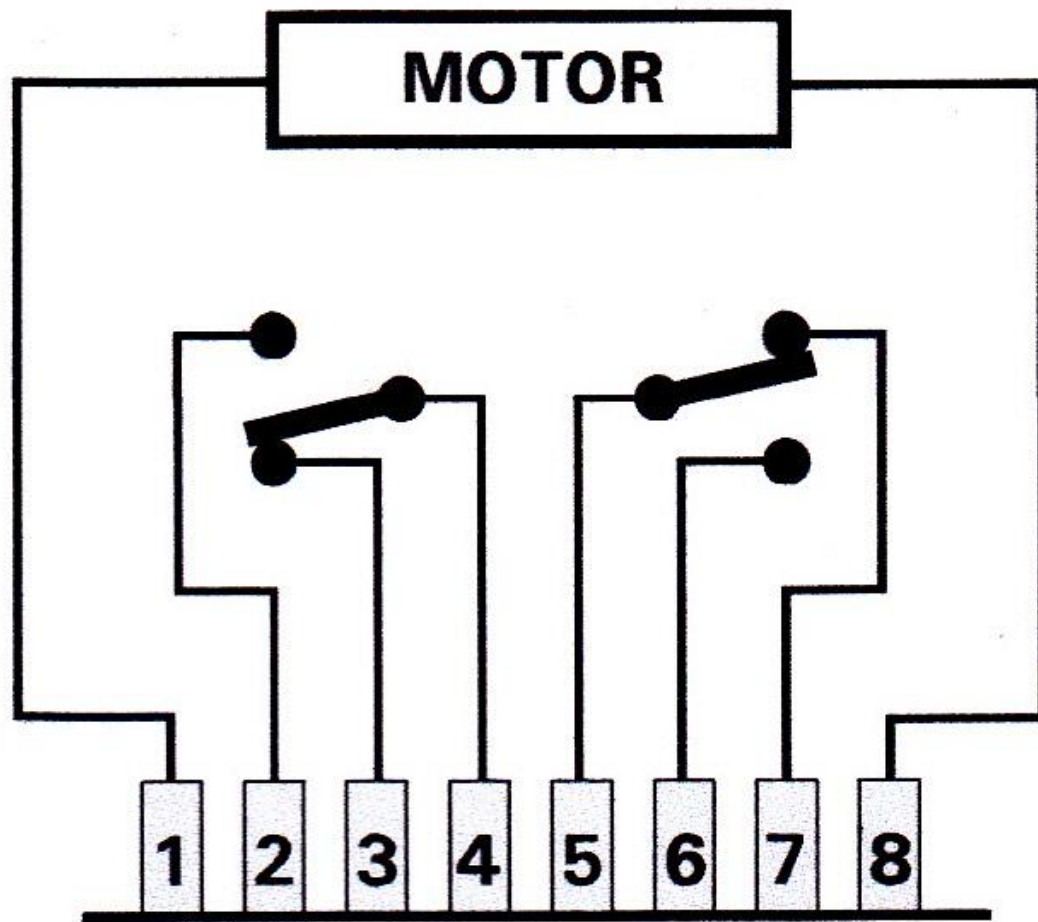

*FIGURE 2.*

# Materials Used

- 2 AC to DC Adapters with 12vdc 500ma output
- 1 SPDT Toggle Switch
- BI-Color LED 3mm or 5mm
- 22AWG Stranded wire
- Terminal Boards
- Crimp on spade connectors


# Sources for Parts

- Mouser
- Digi-Key
- All Electronics
- Jameco


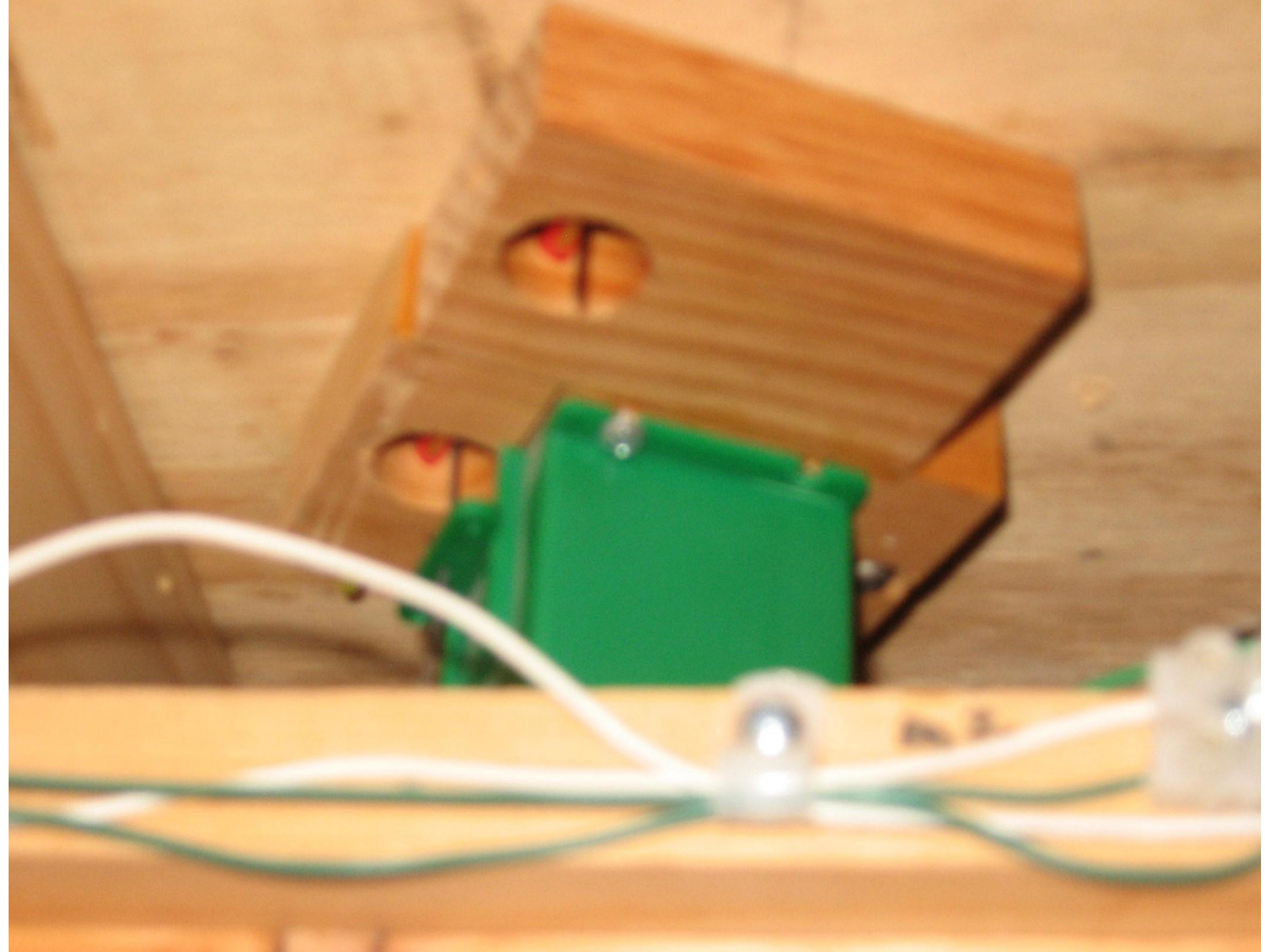
# Additional Reading

- One Turnout Two Controls MR July 2002
- Route Control for Slow motion Motors
- MR Nov. 2000
- Tortoise Tips MR Feb. 2000
- Kalmbach
  - DCC Projects
  - Easy Model Railroad Wiring
  - Basic Electricity & Electronics for Model Railroaders







0101

ed. S  
727;  
califo  
abo  
Class  
CAU  
Will  
hear  
www  
1 R

